

ELE 214
Electronics Laboratory - I

**Multistage Amplifier Design and
Fabrication**

Term Project – Spring 2024

BETÜL ATALAY
2210357078

HACETTEPE UNIVERSITY
Department of
Electrical and Electronics Engineering



PART 1: RESEARCH-CALCULATION	2-6
QUESTION 1	2
QUESTION 2	3
ANALYTICAL CALCULATIONS AND RESULTS	3-6
 PART 2: SIMULATION	 7-11
BUFFER STAGE	7-8
EQUALIZER STAGE	8-9
GAIN STAGE	9-10
MULTISTAGE AMPLIFIER.....	11
 PART 3: PHOTOS OF THE CIRCUIT AND MEASUREMENTS.....	 12-14
 PART 4: CONCLUSION.....	 15
 PART 5: LIST OF REFERENCES	 16-17

PART 1

ANALYTICAL CALCULATIONS AND RESULTS

- **AMPLIFIER:**

An amplifier strengthens weak signals to make them more powerful, with different types including voltage amplifiers, current amplifiers, power amplifiers, and versatile operational amplifiers for tasks like amplification, filtering, and signal conditioning.

- **BUFFER STAGE:**

A buffer stage in an amplifier acts like a signal traffic cop. It keeps the input signal clean (high impedance) and strong (low impedance) for the next stage, preventing unwanted interactions like distortion and ensuring smooth operation.

- **EQUALIZER STAGE:**

The equalizer allows you to adjust the level of different frequencies within that amplified signal. Amplifiers increase the power of the entire audio signal, while equalizers allow adjustment of frequency levels within that amplified signal.

- **GAIN STAGE:**

The gain stage of an amplifier is the section where the signal is amplified, increasing its amplitude to a desired level for further processing or output.

- **MULTISTAGE AMPLIFIER:**

A multistage amplifier is an amplifier circuit that combines multiple single-stage amplifiers for increased overall signal amplification.

- **THE ROLE OF CAPACITOR IN AMPLIFIER DESIGN:**

In amplifier design, capacitors are used for coupling and bypassing: coupling capacitors block DC components while allowing AC signals to pass between stages, and bypass capacitors stabilize the voltage supply and filter out unwanted noise and AC ripple.

- **DIFFERENCES BETWEEN MOSFET AND BJT:**

MOSFET: Voltage-controlled device; having high input impedance; having faster switching speed; more power-efficient; better thermal stability; better suited for digital and high-frequency analog applications; generally easier to integrate into ICs.

BJT: Current-controlled device; having low input impedance; having slower switching speed; less power-efficient; more susceptible to thermal runaway; often preferred for analog amplification due to better linearity and gain characteristics; having more complex fabrication process.

2N2222 BJT:

Used for buffer stage.

Reason for Choice: With a low saturation voltage, the 2N2222 can efficiently operate in the saturation region, ensuring low voltage drops and minimal power loss in the buffer stage. Also it is widely available and provides a high input impedance and low output impedance.

Type: NPN

Transistor Parameters:

- Collector-Emitter Voltage (V_{CEO}): 40V
- Collector Current (I_C): 800mA
- DC Current Gain (h_{FE}): Typically 100-300 at $I_C = 10\text{mA}$
- Collector-Emitter Saturation Voltage ($V_{CE(sat)}$): Typically 0.3V at $I_C = 500\text{mA}$, $I_B = 50\text{mA}$
- Base-Emitter On Voltage ($V_{BE(on)}$): Typically 0.7V at $I_C = 10\text{mA}$

IRF510 MOSFET:

Used for gain stage.

Reason for Choice: The IRF510 boasts a high transconductance (g_m), which translates to significant voltage gain in the amplifier stage. So, it can efficiently amplify the weak signal.

Type: N-channel power MOSFET

Transistor Parameters:

- Drain-Source Voltage (V_{ds}): 100V
- Continuous Drain Current (I_d): 5.6A (at 25°C)
- Gate Threshold Voltage ($V_{gs(th)}$): 2.0V to 4.0V
- $R_{ds(on)}$ (Drain-Source On-Resistance): 0.54Ω (at $V_{gs} = 10\text{V}$, $I_d = 4.0\text{A}$)


ANALYTICAL CALCULATIONS AND RESULTS

All the calculations given below have been made for these frequency values and gain:

- $f_{low} = 780\text{ Hz}$
- $f_{high} = 12200\text{Hz}$
- **Gain** = 8

The calculations that I wrote in handwriting are shown in the pictures below.

I. BUFFER STAGE CALCULATIONS

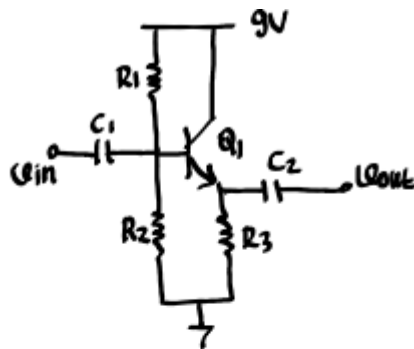

(i) I choose $R_1 = R_2$ for an appropriate biasing.

$$R_{in} = R_1 \parallel R_2 \parallel R_{in-BJT}$$

$$\text{calculating } R_{in-BJT} \approx \beta \cdot R_3$$

$\beta = 100$ from datasheet
and I choose $R_3 = 10k\Omega$

$$\text{So, } R_{in-BJT} = 1M\Omega$$

(ii) Quiescent current for R_1 and R_2 must be higher.
I choose $R_1 = R_2 = 100k\Omega$.

With (i) and (ii):

$$R_{in} \approx 48k\Omega$$

$$(iii) f_c = \frac{1}{2\pi(R_1 \parallel R_2)C_1} \quad ; \quad f_c = 780Hz$$

$$R_1 \parallel R_2 = 50k\Omega$$

$$f_c \leq 780Hz \rightarrow C_1 \geq 4nF$$


I choose $C_1 = 10\mu F$. This makes my buffer stage better.

$$(iv) R_{out} \approx R_1 \parallel \left(\frac{R_2 \parallel R_3}{\beta} \right) \approx 476\Omega$$

(v) With choosing C_2 as $100\mu F$, I observed better buffer stage. This capacitor is responsible for blocking the DC signal and allowing the 100mV AC signal.

Picture 1.1

II. EQUALIZER STAGE CALCULATIONS

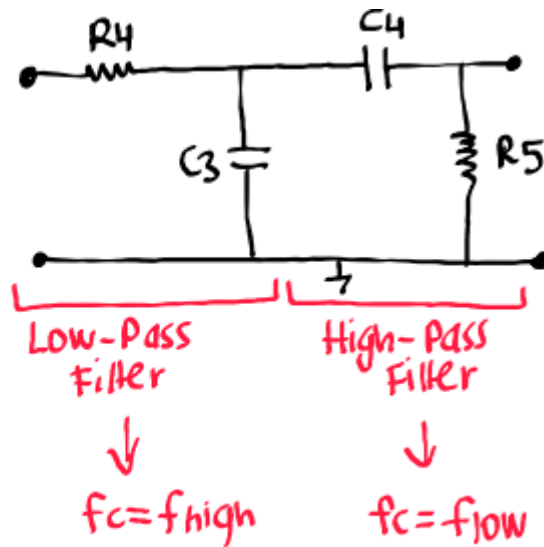

for Low-Pass Filter:

$$12220 \text{ Hz} = \frac{1}{2\pi R_4 C_3} \Rightarrow R_4 = 1.3 \text{ k}\Omega, C_3 = 10 \text{ nF}$$

I choose lower value for C_3 . This makes low-pass filtering better.


for High-Pass Filter:

$$780 \text{ Hz} = \frac{1}{2\pi R_5 C_4} \Rightarrow R_5 = 20.4 \text{ k}\Omega, C_4 = 10 \text{ nF}$$

For R_4 and R_5 values, I use a potentiometer.

Picture 1.2

III. GAIN STAGE CALCULATIONS

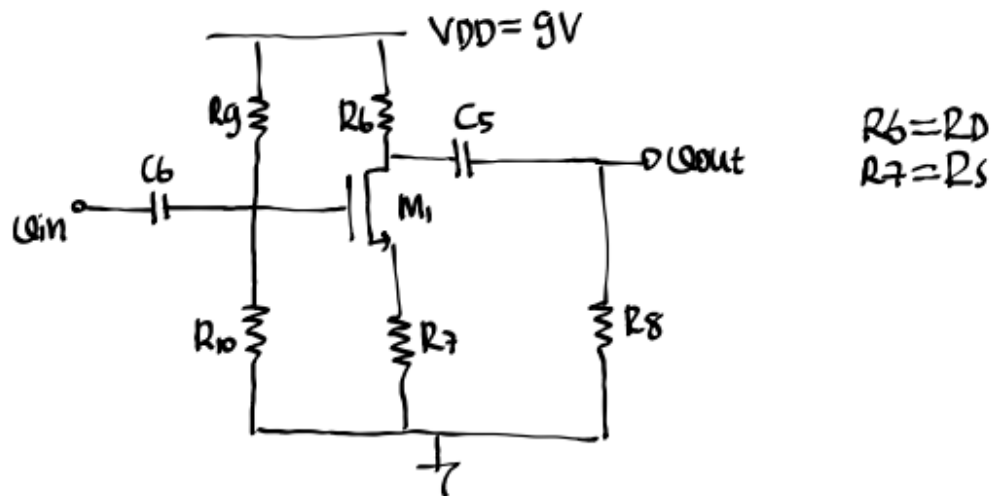

(i) For voltage divider configuration, I choose R_9 and R_{10} values bigger i.e.

$$R_9 = R_{10} = 100 \text{ k}\Omega$$

(ii) Assume $I_D \approx 6 \text{ mA}$; $2\text{V} \leq V_{TH} \leq 4\text{V}$

$$\text{Choose } V_{TH} = 3\text{V}$$

$$K = 8.25 \times 10^{-3} \text{ A/V}^2$$

$$I_D = K(V_{GS} - V_{TH})^2 \Rightarrow V_{GS} = 3.846\text{V}$$

(iii) For $V_D \approx 3\text{V}$,

$$R_D = \frac{V_D}{I_D} \approx 1 \text{ k}\Omega$$

$$(iv) |A_{vL}| = \frac{R_D}{\frac{1}{g_m} + R_S} \approx \frac{R_D}{R_S} = 8 \rightarrow R_S = 125 \Omega$$

Picture 1.3

PART 2

1) BUFFER STAGE SIMULATION



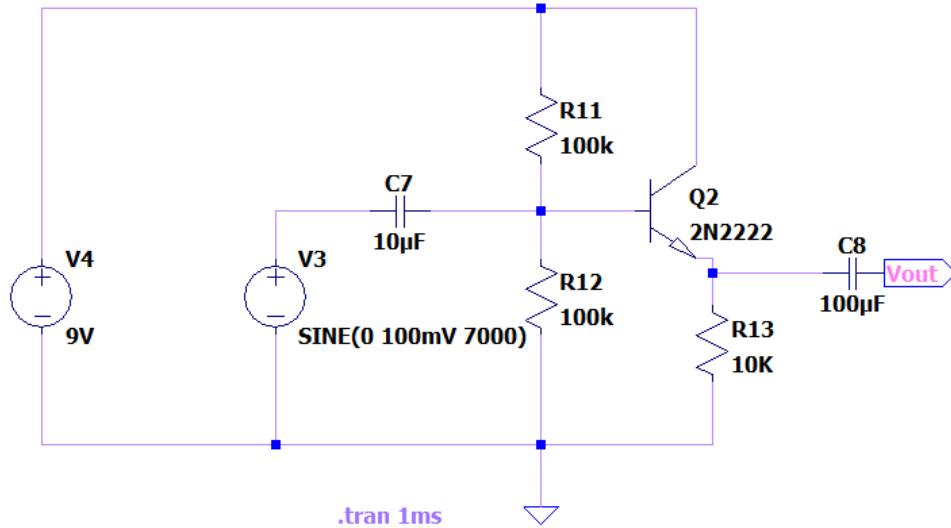


Figure 2.1

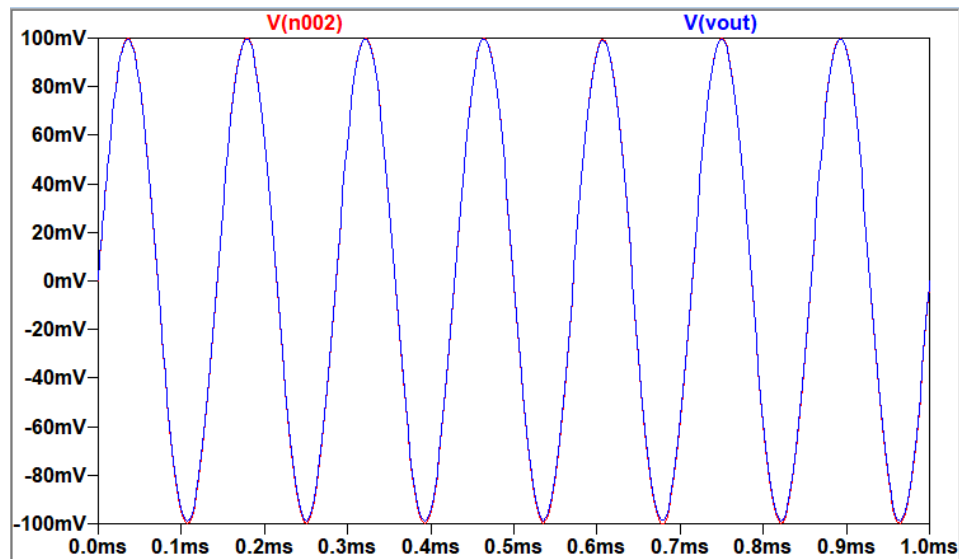

Graph 2.1

With choosing appropriate component values, I aimed that the gain should equal to 1. As seen in the Graph 2.1, Vout and Vin is almost equal and $A_v \approx 1$.

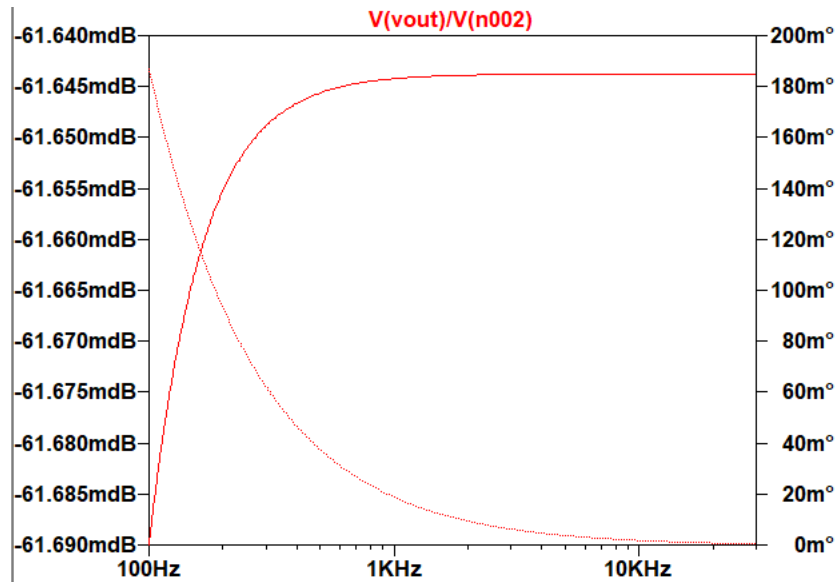

Graph 2.2

Graph 2.2 shows the frequency response of the buffer stage.

2) EQUALIZER STAGE SIMULATION



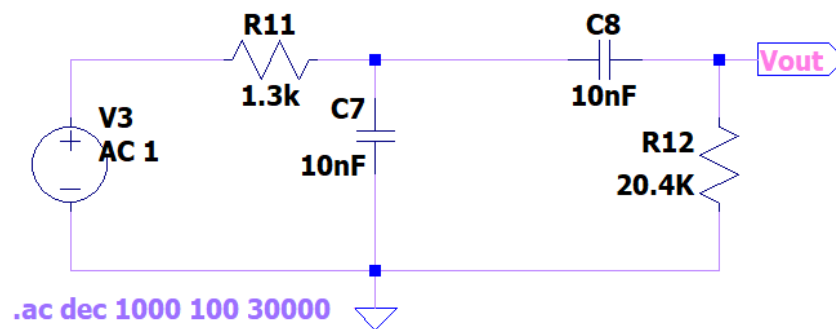


Figure 2.2

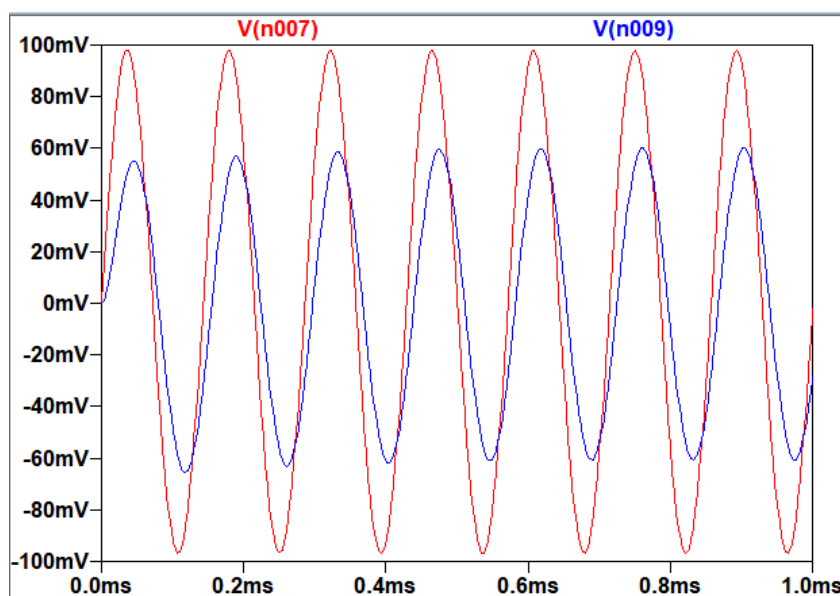

Graph 2.3

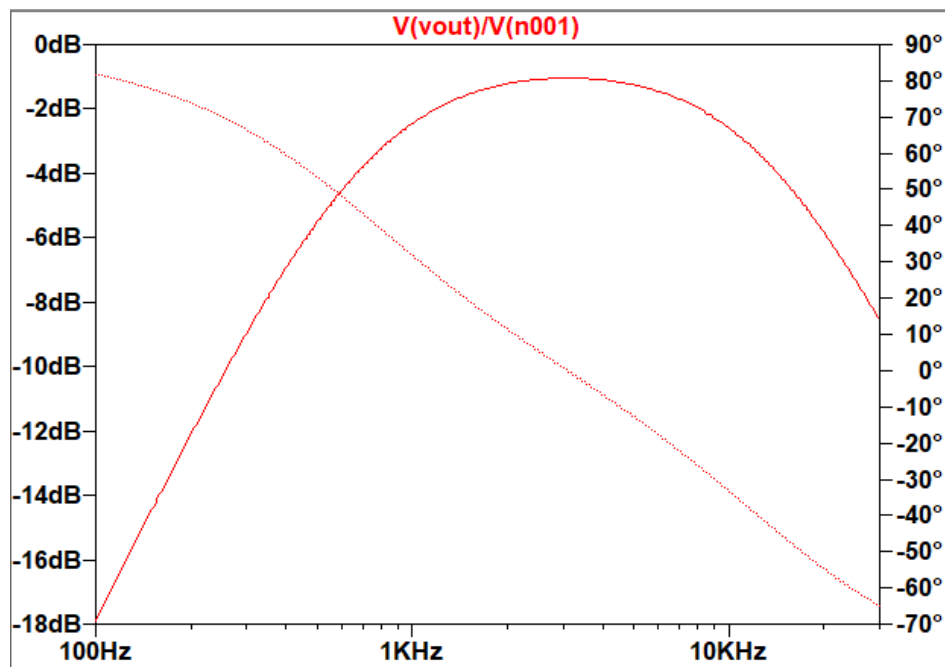

Graph 2.4

As seen in Figure 2.2, I set my equalizer circuit with bandpass filter. First part is low-pass filter which arranged for $f_{\text{high}} = 12200\text{Hz}$. Second part is high-pass filter which arranged for $f_{\text{low}} = 780\text{Hz}$. After the low-pass filter my gain stays constant, but after high-pass filter my gain decreases as expected as shown Graph 2.3. Red line indicates the output of the buffer stage and the blue one indicates the output of equalizer stage.

I tried different frequency values to test my equalizer stage. I observed that the gain decreases for frequencies which is lower than $f_{\text{low}} = 780\text{Hz}$ and higher than $f_{\text{high}} = 12200\text{Hz}$. Graph 2.4 shows the bandpass filters frequency response and there exists a 80-degree phase difference within the bandwidth

3) GAIN STAGE SIMULATION



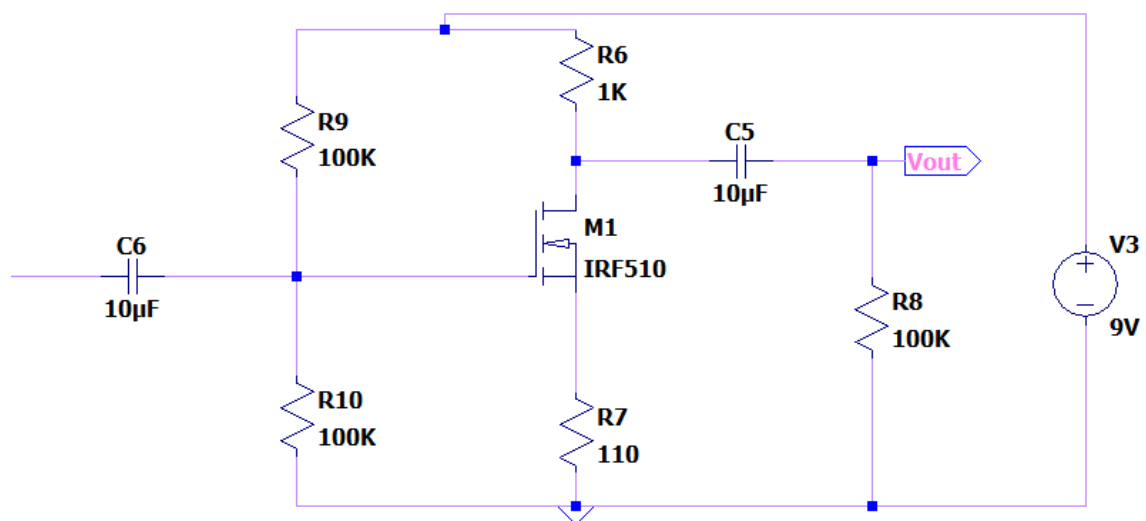


Figure 2.3

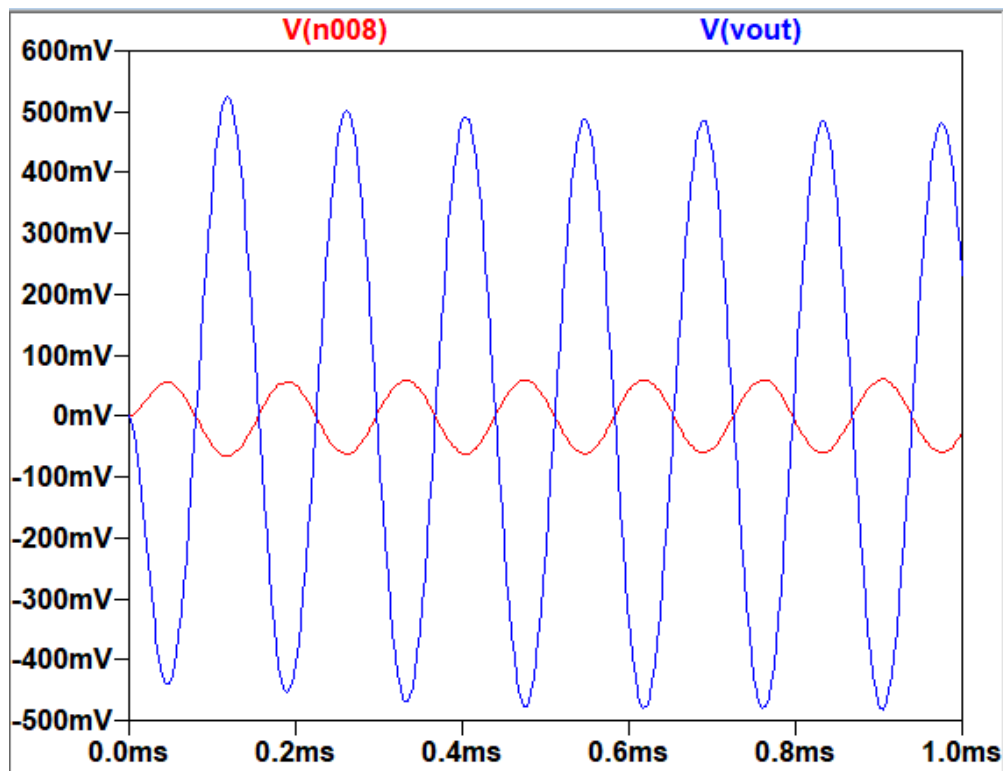

Graph 2.5

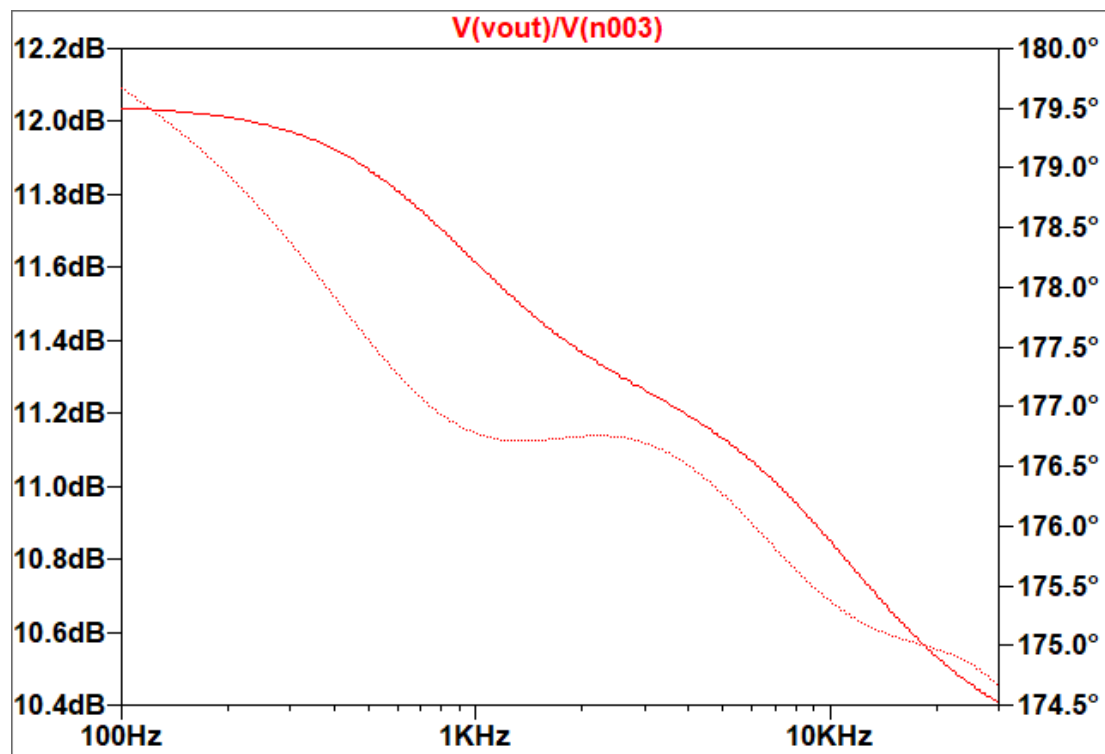

Graph 2.6

My gain must be 8. As seen in the Graph 2.5, input comes from the equalizer stage. It is approximately 60Mv. Output is observed from the C5 and its value is approximately 480Mv.

$$\text{Gain} = V_{\text{out}}/V_{\text{in}} = 480\text{mV} / 60\text{mV} = 8.$$

4) MULTISTAGE AMPLIFIER SIMULATION


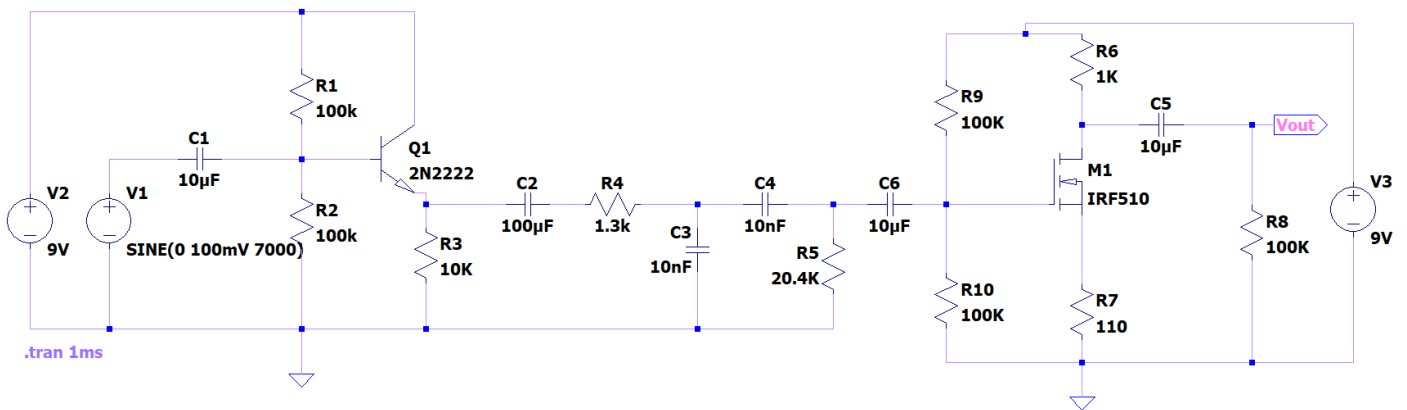


Figure 2.4

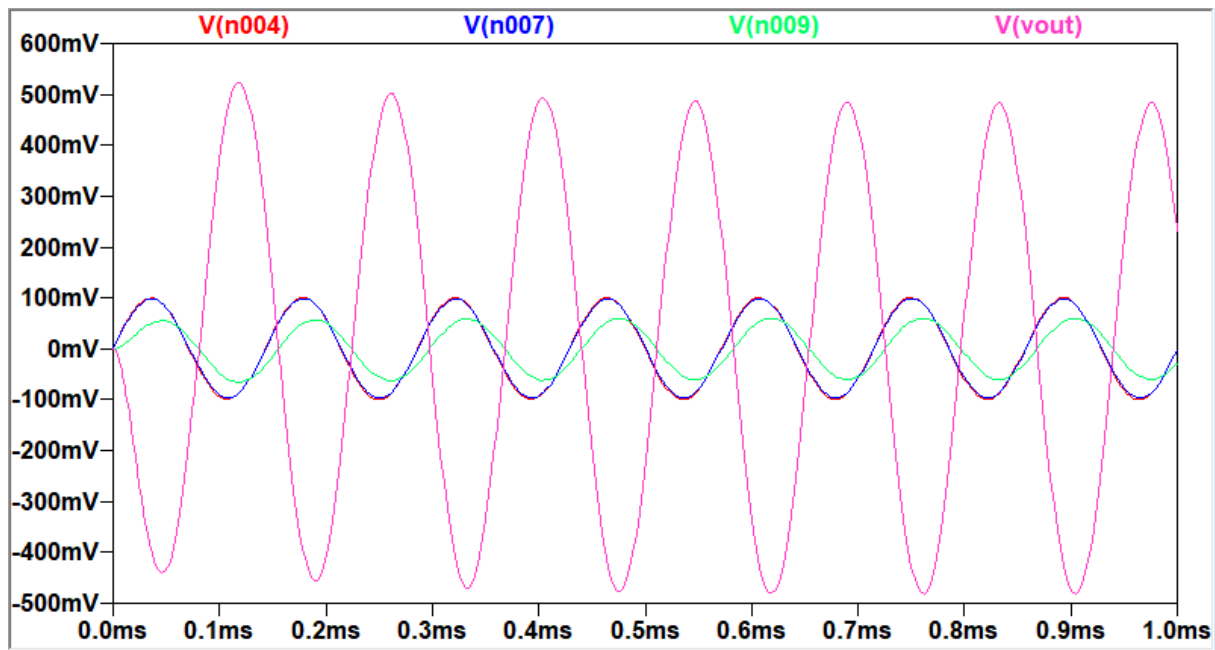


Graph 2.7


In the Graph 2.7, V(n004) (red line) indicates the input signal 100mV, V(n007) (blue line) is the output of the buffer stage and it is almost 100 mV, V(n009) (green line) is the output of the equalizer stage and it is 60 mV, and the last one V(vout) (pink line) is the output of the gain stage and approximately 480 – 500 mV.

PART 3

PHOTOS OF THE CIRCUIT ON BREADBOARD AND MEASUREMENTS

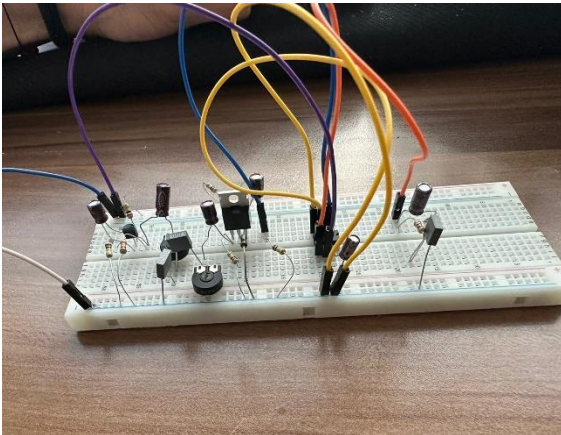


Picture 3.1

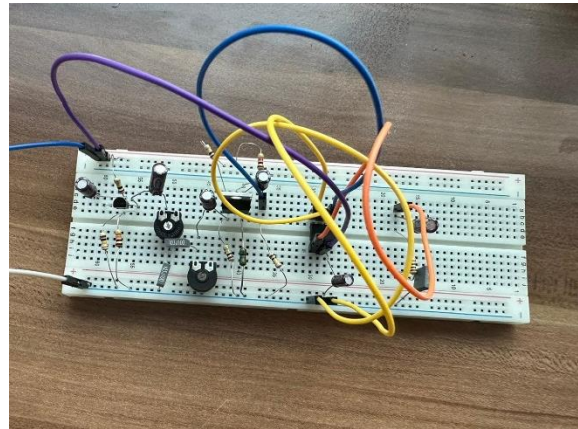

Picture 3.2


BUFFER STAGE:

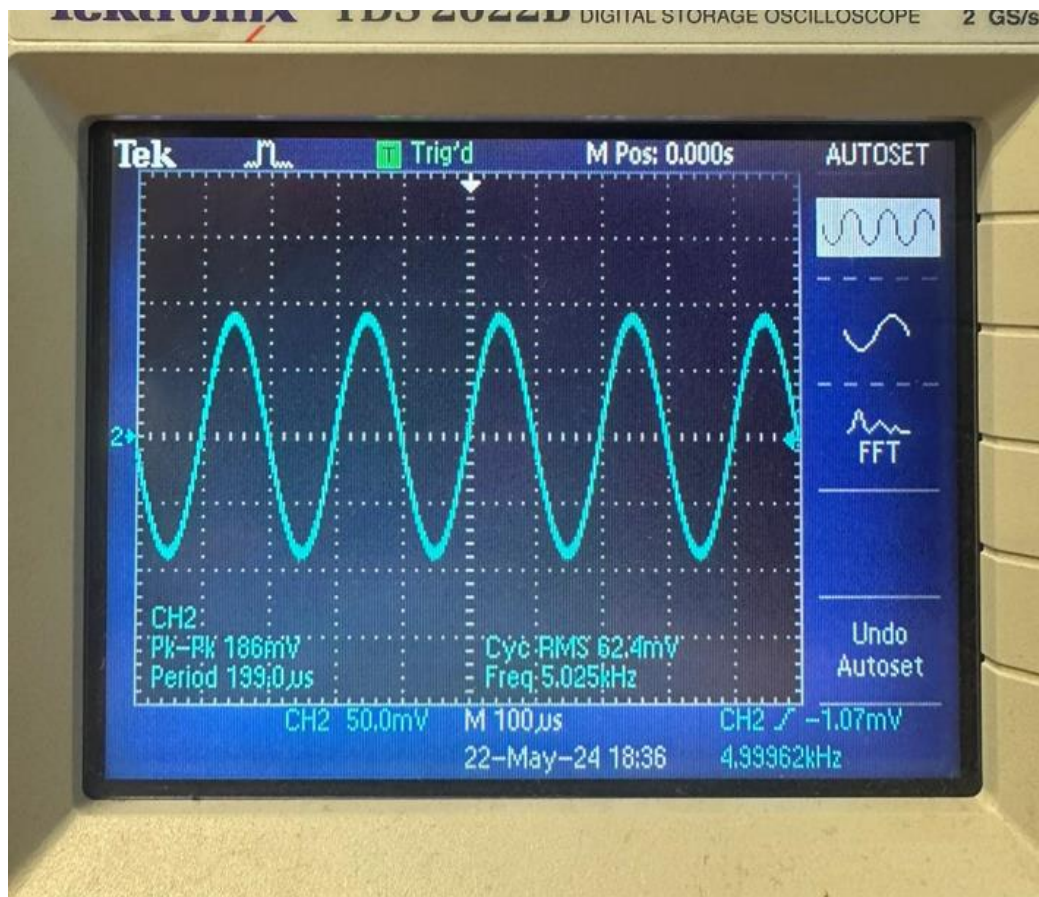

Picture 3.3


EQUALIZER STAGE:

- $f=200\text{Hz}$:

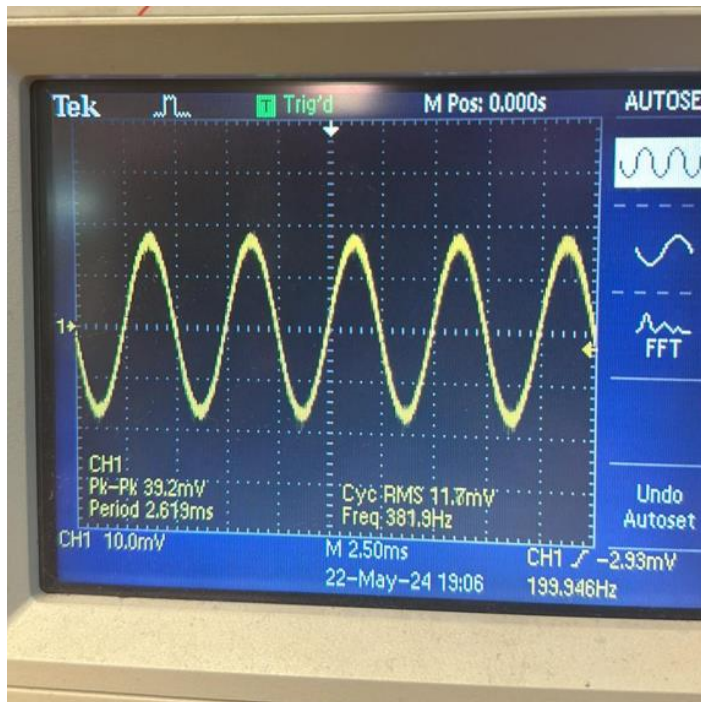


Picture 3.4

- $f = 2\text{KHz}$:

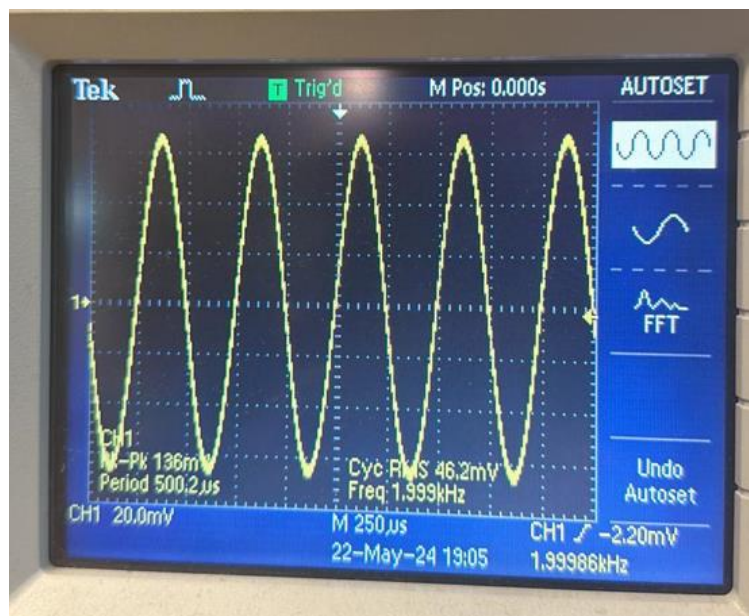


Picture 3.5

- $f=20\text{kHz}$:

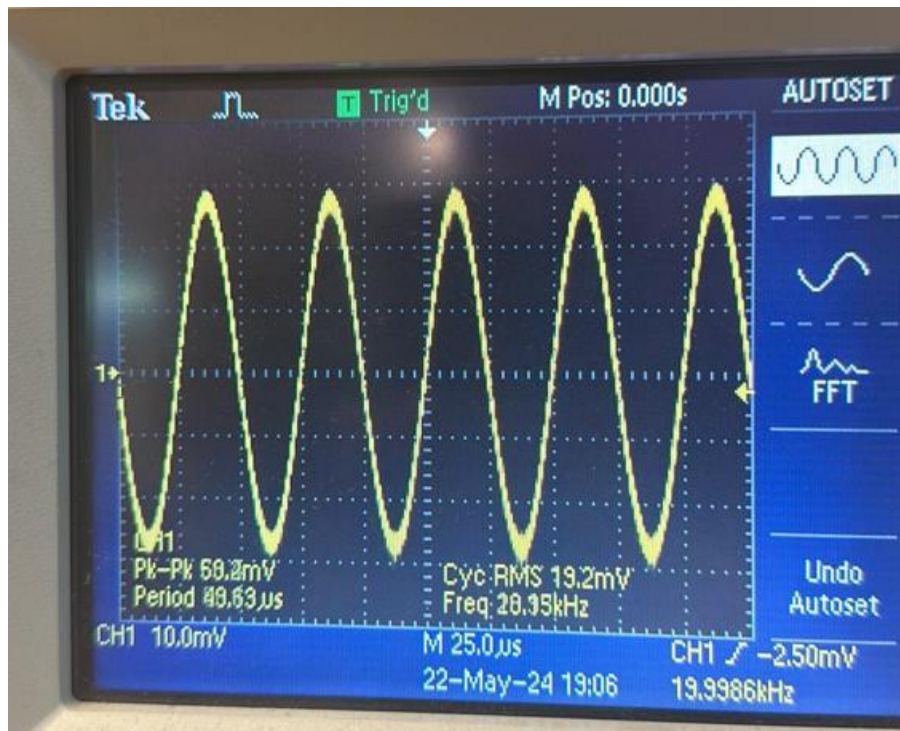

Picture 3.6

GAIN STAGE:

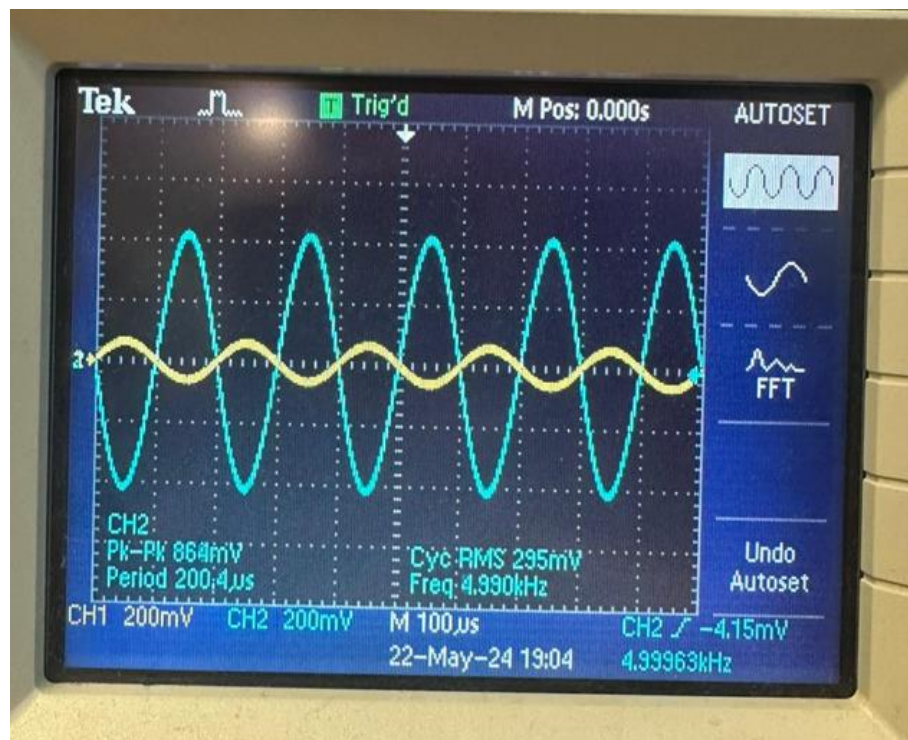

Picture 3.7

CONCLUSION

In this project, I designed a multistage amplifier consisting of a buffer stage, an equalizer stage, and a gain stage. In the buffer stage, I used a 2N2222 BJT to fix the gain at 1. In the equalizer stage, I used a passive bandpass filter to adjust the frequency range, with the lowest frequency set at 780 Hz and the highest at 12.200 Hz. Finally, for the gain stage, I used an IRF510 MOSFET to achieve a gain of 8. I successfully completed all these stages as expected. Although there was some gain loss in the equalizer stage, my gain stage was able to amplify the output of this stage effectively. I tested my design in the electronics laboratory, and both my simulations and calculations were accurate.

LIST OF REFERENCES

General Amplifier Information:

- Source: Sedra, A. S., & Smith, K. C. (1998). Microelectronic Circuits (4th ed.). Oxford University Press.
- Source: Boylestad, R. L., & Nashelsky, L. (2006). Electronic Devices and Circuit Theory (10th ed.). Pearson Education.

Buffer Stage:

- Source: Horowitz, P., & Hill, W. (2015). The Art of Electronics (3rd ed.). Cambridge University Press.
- Source: Malvino, A. P., & Bates, D. J. (2016). Electronic Principles (8th ed.). McGraw-Hill Education.

Equalizer Stage:

- Source: Self, D. (2009). Audio Equalization: Analog and Digital Techniques. Newnes.
- Source: Watkins, J. (1995). High-Fidelity Audio Equipment: Design, Construction, and Use. Radio Society of Great Britain.

Gain Stage:

- Source: Millman, J., & Halkias, C. C. (1972). Integrated Electronics: Analog and Digital Circuits and Systems. McGraw-Hill.
- Source: Gray, P. R., Hurst, P. J., Lewis, S. H., & Meyer, R. G. (2009). Analysis and Design of Analog Integrated Circuits (5th ed.). John Wiley & Sons.

Multistage Amplifier:

- Source: Razavi, B. (2000). RF Microelectronics. Prentice Hall.
- Source: Franco, S. (2014). Design with Operational Amplifiers and Analog Integrated Circuits (4th ed.). McGraw-Hill Education.

Role of Capacitor in Amplifier Design:

- Source: Roberge, J. K. (1975). Operational Amplifiers: Theory and Practice. John Wiley & Sons.
- Source: Van Valkenburg, M. E. (1982). Analog Filter Design. Holt, Rinehart and Winston.

Differences Between MOSFET and BJT:

- Source: Neamen, D. A. (2009). Microelectronics: Circuit Analysis and Design (4th ed.). McGraw-Hill Education.
- Source: Streetman, B. G., & Banerjee, S. (2006). Solid State Electronic Devices (6th ed.). Pearson Prentice Hall.

2N2222 BJT:

- Source: Fairchild Semiconductor. (2015). 2N2222 Datasheet. Retrieved from Fairchild Semiconductor

- Source: NXP Semiconductors. (2012). 2N2222; 2N2222A NPN Switching Transistor. Retrieved from NXP Semiconductors

IRF510 MOSFET:

- Source: Vishay Siliconix. (2015). IRF510, SiHF510 N-Channel Power MOSFET. Retrieved from Vishay
- Source: International Rectifier. (2001). IRF510 Datasheet. Retrieved from International Rectifier